


# PicPop Power Distribution Plan


Single power supply feeding an intermediate power board that provides 12V for the monitor and 5V for the Radxa and camera.

## OPTION 1: USB-C PD Power Supply


Uses a USB-C Power Delivery brick with a PD trigger to negotiate 12V.

### System Diagram (Option 1)

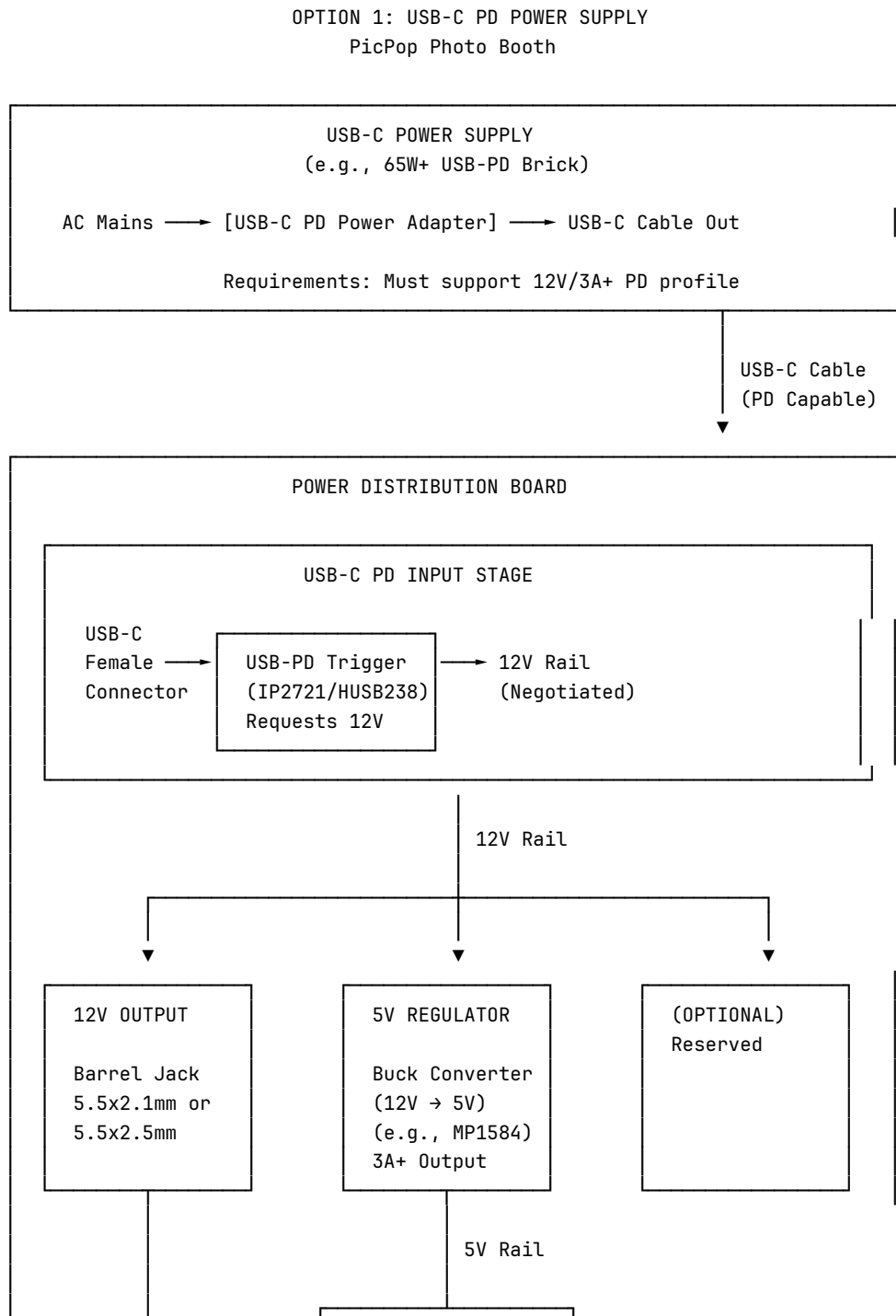

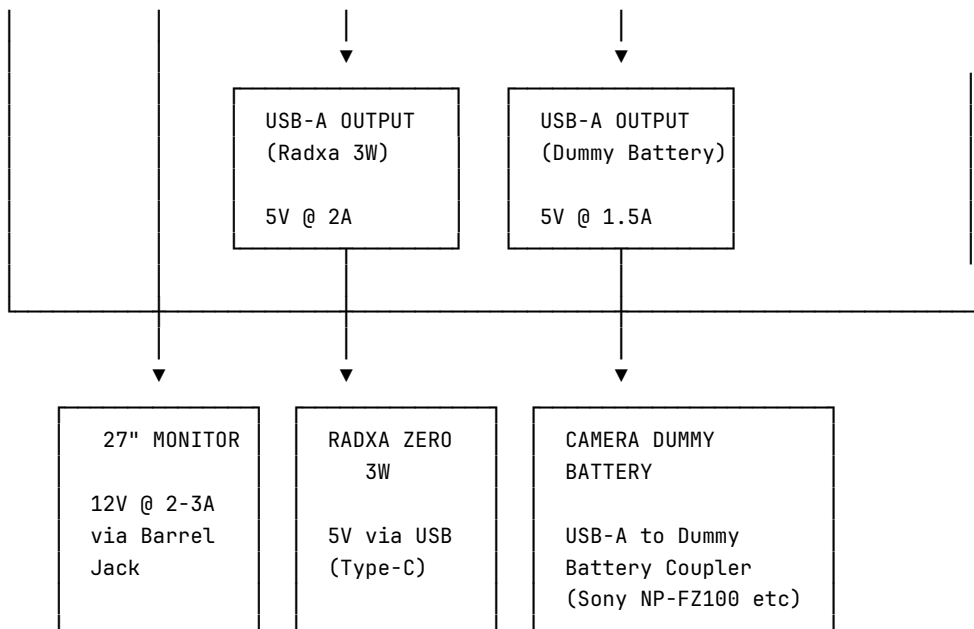

### Wiring Summary (Option 1)

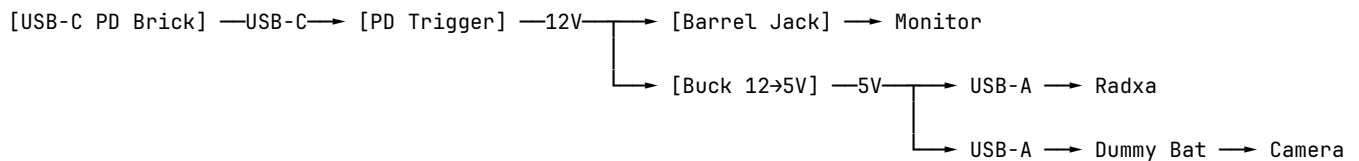

### USB-C PD Trigger Options

Module	Price	Notes
IP2721	\$2-5	Simple fixed 12V trigger
HUSB238	\$3-6	Programmable, I2C control
CH224K	\$2-4	Popular, configurable via resistors

### Option 1 Pros/Cons


Pros	Cons
Compact, portable power brick	Requires PD trigger module
USB-C is universal/modern	Not all bricks support 12V profile
Easy to find replacement bricks	More complex distribution board
Can double as laptop charger	PD negotiation adds failure point

## OPTION 2: 12V DC Power Supply

Uses a traditional 12V DC barrel jack power supply (like a laptop charger).

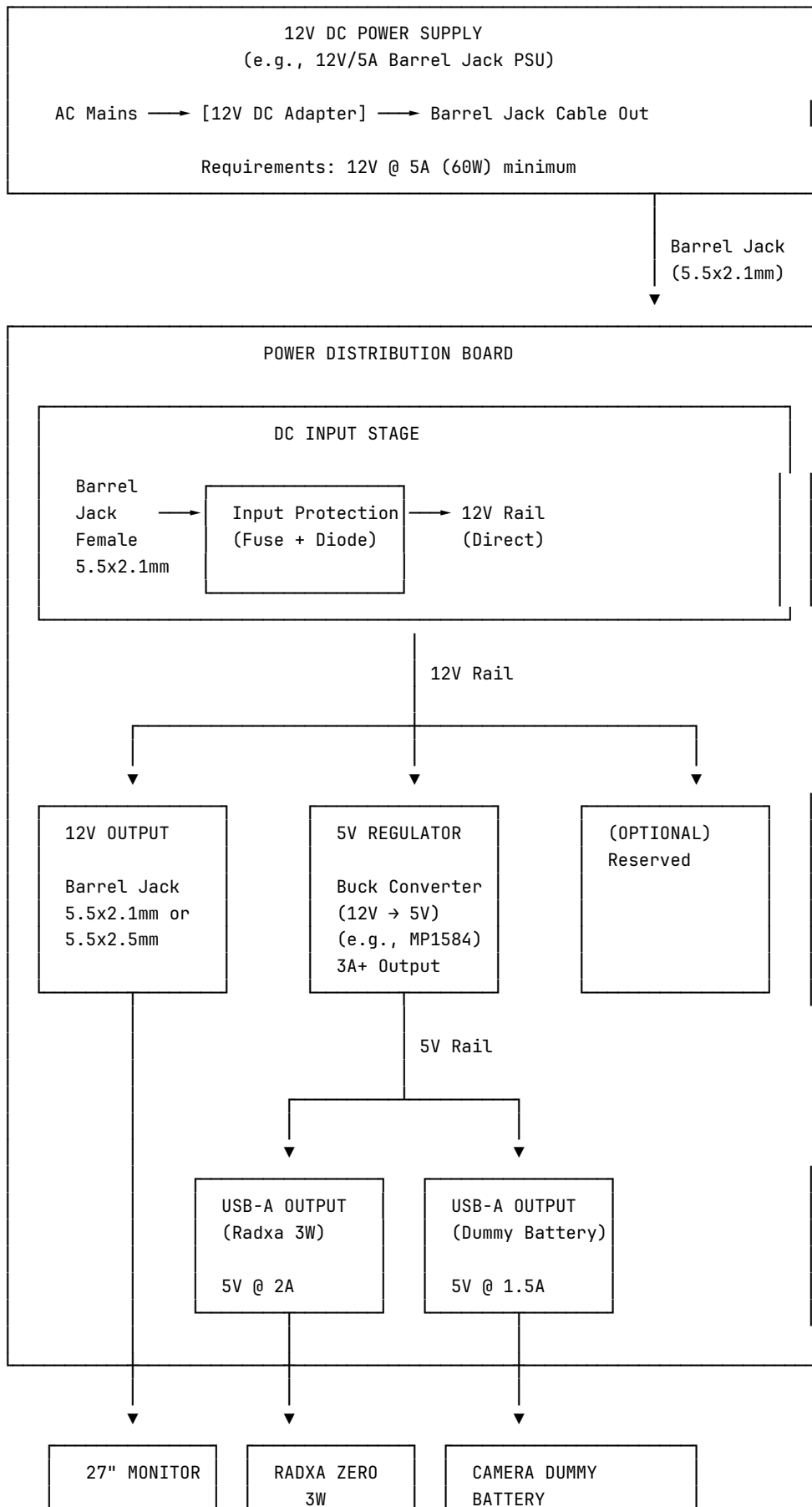
### System Diagram (Option 2)

OPTION 2: 12V DC POWER SUPPLY  
PicPop Photo Booth



12V @ 2-3A via Barrel Jack	5V via USB (Type-C)	USB-A to Dummy Battery Coupler (Sony NP-FZ100 etc)
----------------------------------	------------------------	--

### Wiring Summary (Option 2)

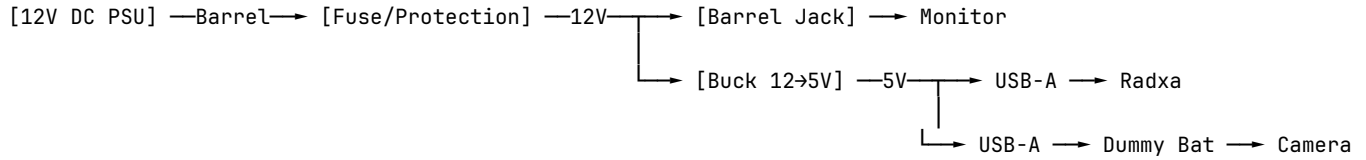

### Option 2 Pros/Cons

Pros	Cons
Simple, no PD negotiation needed	Bulkier power supply
Cheap and widely available	Less portable
Direct 12V, fewer failure points	Need specific voltage PSU
Easy to find high-current units	Extra cable/brick to carry

## Shared Components (Both Options)

### Buck Converter (12V to 5V)

Module	Price	Max Current	Notes
MP1584	\$1-3	3A	Compact, good efficiency
LM2596	\$2-4	3A	Adjustable output
Mini360	\$1-2	1.8A	Very compact (single device only)

### Barrel Jack Connector (Monitor Output)

- Check your monitor's barrel jack size!
- Common sizes: 5.5x2.1mm or 5.5x2.5mm
- Verify polarity: Usually center-positive

## Power Budget

Component	Voltage	Current	Power
27" Monitor	12V	2-3A	24-36W
Radxa ZERO 3W	5V	2A (peak)	10W
Dummy Battery (Camera)	5V	1.5A	7.5W
<b>Total</b>			<b>42-54W</b>

### Recommendation:

- Option 1: Use a 65W+ USB-PD power supply (must support 12V profile)
- Option 2: Use a 12V/5A (60W) DC adapter minimum

## Key Considerations

1. **Option 1 - USB-PD Negotiation:** The PD trigger module must successfully negotiate 12V. Verify your brick supports the 12V PD profile (not all do - many jump from 9V to 15V or 20V).
  2. **Option 2 - Voltage Tolerance:** Cheap 12V adapters may output 12.5-13V. This is fine for monitors and buck converters but verify your monitor's tolerance.
  3. **Barrel Jack Sizing:** Measure your monitor's barrel jack carefully. 5.5x2.1mm and 5.5x2.5mm look nearly identical but won't interchange properly.
  4. **5V Rail Current:** The buck converter handles combined load of Radxa (~2A peak) + dummy battery (~1.5A). Use a converter rated for 4-5A minimum.
  5. **Heat Dissipation:** The buck converter will dissipate ~3.5W as heat at full load. Ensure adequate ventilation or add a small heatsink.
  6. **Input Protection (Option 2):** Add a fuse (5A) and reverse polarity diode to protect against wrong adapter or shorts.
- 

## Recommendation

**Option 2 (12V DC) is simpler and more reliable** for a stationary photo booth:

- No PD negotiation complexity
- Cheaper overall
- Easier to troubleshoot
- More headroom on current capacity

**Option 1 (USB-C PD) is better if:**

- Portability is important
- You want to use one charger for multiple devices
- You already have a compatible USB-PD brick